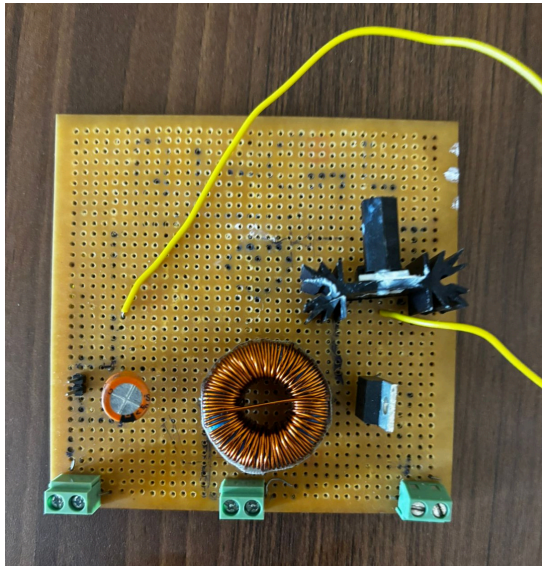


Problem Statement


To implement a DC-DC boost converter and observe its performance by analyzing output waveforms in CCM and DCM using an oscilloscope.

Batch: G1-B4


Roll no: 240002013, 240002006 , 240002040, 240002035



Soldered Boost Converter Circuit

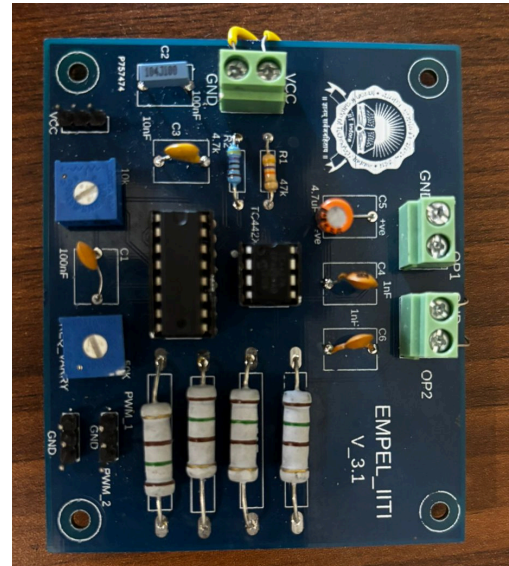

Gate Driver PCB

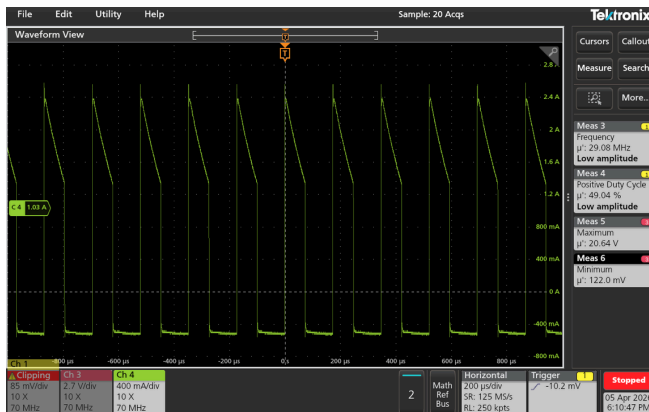


Diode current (CCM)



Diode current (DCM)



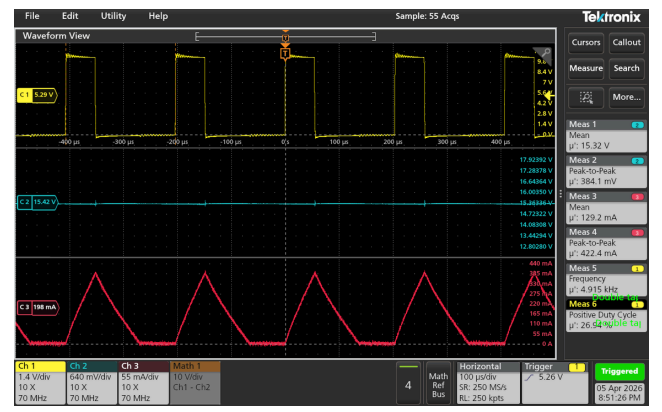Inductor current and output Voltage (CCM)



Inductor current and output Voltage (DCM)

DCM Resistance = 214 ohms

Dcm and CCM simulation

Output voltage simulation